


## Unit-II:- Combinational Circuits.

Combinational Logic Circuits: Adders & Subtractors, Multiplexers, Demultiplexers, Encoders, Decoders, Programmable Logic Devices.

### Adders:-
 
#### Half Adder:-

A combinational circuit that performs addition of two bits is called a half adder.



$x \backslash y$	0	1
0		1
1	1	

$$\text{Sum} = xy' + x'y$$

$x \backslash y$	0	1
0		
1		1


$$\text{Carry} = xy$$

$x$	$y$	$C$	$S$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0



#### Implementation of half adder:-

$$S = x \oplus y = xy' + x'y$$

$$C = xy$$

 


(or)

  
 
## Full Adder:-

A combinational circuit that performs the addition of three bits (2-significant bits and previous carry) is called a full adder.

Two half adders can be employed to implement full adder.



	x	y	z	Carry	Sum
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	1

$$\text{Sum} = x'y'z + x'y z' + xy'z' + xyz$$


$$\text{Carry} = xz + yz + xy$$


$$\begin{array}{r} 101 \\ 111 \\ \hline 112 \end{array} \quad \begin{array}{r} 111 \\ 011 \\ \hline 42 \end{array} \quad \begin{array}{r} 111 \\ 110 \\ \hline 117 \end{array}$$

## Implementation of full adder:-



$$\text{Sum} = x'y'z + x'y z' + xy'z' + xyz$$

$$\text{Carry} = xz + yz + xy$$

 

 

  Implementation of full adder using Two half adders:



$$\text{Sum} = (x \oplus y) \oplus z$$

$$= (xy' + x'y) \oplus z$$

$$= (xy' + x'y)z' + (xy' + x'y)z$$

$$= xy'z' + x'yz' + (xy' + x'y)z$$

$$\therefore \text{Sum} = xy'z' + x'yz' + xy'z + x'yz$$



$$\text{Carry} = (x \oplus y) \cdot z + xy$$

$$= (xy' + x'y)z + xy$$

$$= xy'z + x'yz + xy$$

$$= xy'z + x'yz + xy(z + z')$$


$$= xy'z + x'yz + xyz + xyz'$$

$$\text{Carry} = xz + yz + xy$$

Karnaugh Map for Carry =  $xz + yz + xy$

	$yz$	00	01	11	10
$x$	0			1	
	1		1	1	1

 Binary Adder (or) Ripple Carry Adder on 4-bit adder:-



Subscript	3	2	1	0	
i/p carry	0	1	1	0	C <sub>i</sub>
Augend	1	0	1	1	A <sub>i</sub>
Addend	0	0	1	1	B <sub>i</sub>
Sum	1	1	1	0	S <sub>i</sub>
o/p carry	0	0	1	1	C <sub>i+1</sub>

The above figure shows the inter connection of 4 full adder circuits to provide 4-bit binary ripple carry adder. The carries are connected in a chain through the full adders. The input carry

to the adder is  $C_0$  and it ripples through the full adder to the O/p carry  $C_4$ .

The 'S' outputs generates the required sum bits. An  $n$ -bit adder requires  $n$ -full adders with each o/p carry connected to the input carry of next higher adder full adder.

### Carry Propagation:-

The total propagation time equal to the propagation delay of typical gate times the number of gate levels in the circuit. The longest propagation delay time in an adder is the time it takes the carry to propagate through the full adder.

Let the input carry  $C_3$  does not settle to its final value until  $C_2$  is available from previous stage.

Similarly,  $C_2$  has to wait for  $C_1$  and so on down to  $C_0$ . Thus, only after the carry propagates and ripples through all stages will the last output  $S_3$  and carry  $C_4$  settle to their final correct value.


So the carry propagation time is an important attribute of the adder because it limits the speed with which two numbers are added.

---
 
### Carry look ahead logic / Generator:-

There are several techniques for reducing the carry propagation time in a parallel adder. The most widely used technique employs the principle of carry look ahead logic.





$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$


$$S = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$


put  $i=0$ ,  $C_1 = G_0 + P_0 C_0$

put  $i=1$ ,  $C_2 = G_1 + P_1 C_1$   
 $= G_1 + P_1 (G_0 + P_0 C_0)$   
 $= G_1 + P_1 G_0 + P_1 P_0 C_0$

 put  $i=2$ ,  $C_3 = G_2 + P_2 C_2$   
 $= G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_0)$   
 $= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$



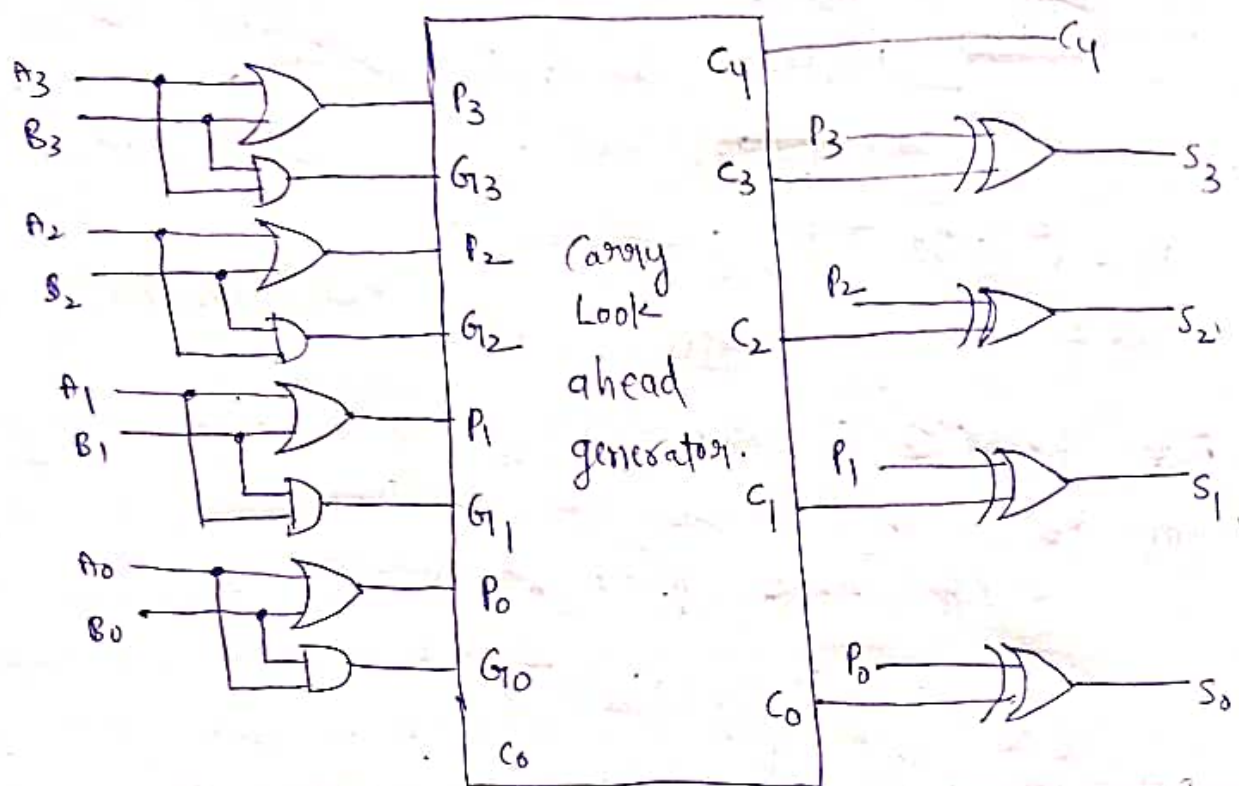
# 4-bit binary adder with carry look ahead generator Speed Binary Adder:-


 
## Half Subtractor:-

The two inputs for half subtractor are  $x$  and  $y$  from the minuend and the subtrahend,  $D$  is the difference output and  $B$  is the borrow o/p.



$x$	$y$	$B$	$D$
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

for difference,



$x \backslash y$	0	1
0		①
1	①	

$$D = xy' + x'y = x \oplus y$$

for borrow,

$x \backslash y$	0	1
0		⊕
1		

$$B = x'y$$

  

### Full Subtractor:

A full subtractor has three inputs and two outputs.  $x, y$  and  $z$  are the inputs to be subtracted in which  $z$  represents borrow from the next stage.  $D$  and  $B$  are the outputs.



for difference

$x \backslash yz$	00	01	11	10
0		1		1
1	1		1	

$x$	$y$	$z$	$B$	$D$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$D = xy'z' + x'y'z + xy'z + x'y'z = x \oplus y \oplus z$$

$$D = \Sigma (1, 2, 4, 7)$$

for borrow,

$x \backslash yz$	00	01	10	11
0		1	1	1
1			1	



$$B = x'y + x'z + yz$$

$$\frac{010}{x'y}$$

$$\frac{001}{x'z}$$


$$\frac{011}{yz}$$



  
 
### Binary Subtractor (an Adder / Subtractor Circuit)

The addition and subtraction operations can be combined into one circuit. In this mode input 'M' controls the operation, when  $M=0$  the circuit is an adder, when  $M=1$  the circuit becomes a subtractor.



Overflow (if 4).

### Overflow :-


When two numbers with 'n' digits each are added, sum is a number occupying 'n+1' digits, we say that an overflow occurred.

Overflow is a problem in digital computers because the number of bits that hold the number is finite and a result that contains ' $n+1$ ' bits can ~~be~~ not be accommodated by an ' $n$ ' bit word, when overflow occurs a corresponding flip flop is set in the above binary adder subtractor that can then be checked by the user.


### Multiplexer (MUX):

- (i) A multiplexer is a combinational circuit that selects binary information from one of many i/p lines and directs it to a single o/p line.
- (ii) The selection of a particular i/p line is controlled by set of selection lines.
- (iii) Normally there are  $2^n$  input lines and ' $n$ ' selection lines whose bit combination determine which i/p is selected.

### 2-4 MUX:

 

(or)

 


Function Table

S	Y
0	$I_0$
1	$I_1$

## 4-1 MUX:

Function Table

$S_1$	$S_0$	o/p
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

 


## Quadruple 2-1 MUX:

$$2^n = 2^1$$

$$n=1$$

$E$	$S$	o/p
1	X	0
0	0	A
0	1	B

 



## Boolean function Implementation:-

Boolean function of ' $n$ ' variables with a multiplexer that has ' $n$ ' selection inputs and  $2^n$  data inputs '1' for each min term. For implementing a boolean function of ' $n$ ' variables with a multiplexer that has ' $n-1$ ' selection inputs and  $2^{n-1}$  data inputs.

The first ' $n-1$ ' variables of the function are connected to the inputs of the multiplexer. The remaining single variable of the function is used for the data inputs if the single variable is denoted by ' $z$ ', each data input of the multiplexer will be  $z, \bar{z}, 1$  (or)  $0$ .

① Implement the boolean function


$F(x, y, z) = \sum (1, 2, 6, 7)$  with a multiplexer.

Sol:- Here,  $n=3$ . = no. of variable (3 variables).

$$2^{n-1} = 2^{3-1} = 2^2 = 4 \text{ inputs.}$$

$$n-1 = 3-1 = 2 \text{ selection lines.}$$

$S_1$	$S_0$	$z$	$F$
$x$	$y$		
0	0	0	0
0	0	1	1 $F=2$
0	1	0	1 $F=3$
0	1	1	0
1	0	0	0 $F=0$
1	0	1	0
1	1	0	1 $F=1$
1	1	1	1

 

② Implement the boolean function


$F(A, B, C, D) = \sum (1, 3, 4, 11, 12, 13, 14, 15)$  with a multiplexer.

Soln Here,  $n = 4$

$$2^n - 1 = 2^{4-1} = 2^3 = 8 \text{ inputs}$$

$$n - 1 = 4 - 1 = 3 \text{ selection lines}$$


$s_2$	$s_1$	$s_0$			
A	B	C	D		F
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = D$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	1	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

 

### Three State Gates:-

A multiplexer can be constructed with three state gates. Two of the states are signals equivalent to logic-1 and logic-0 in a conventional gate.

The third state is high impedance state.

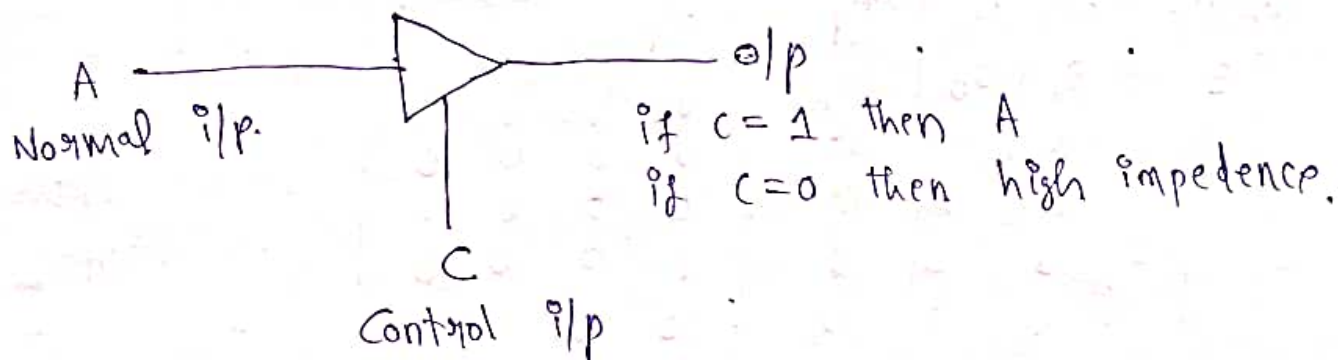


Q Draw 2:1 multiplexer with 3-state gate.

sol:  $n = \text{inputs} = 2$   
 $2^n = 2 = 2^1$

$(n=1)$  selection line

Selection line	o/p
$S_0$	$Y$
0	$I_0$
1	$I_1$

 

### Demultiplexer:-


A demultiplexer is a circuit that receives information on single line and transmits this on one of the  $2^n$  output lines. The selection of specific output lines is controlled by the value of 'n' selection lines.



① Draw the 1:4 de-multiplexer.


Sol<sup>n</sup>  $2^n = 4 = 2^2$

$n=2$

 

Function Table


Enable	selection		i/p	o/p.			
E	S <sub>1</sub>	S <sub>0</sub>	D <sub>in</sub>	y <sub>0</sub>	y <sub>1</sub>	y <sub>2</sub>	y <sub>3</sub>
0	X	X	X	0	0	0	0
1	0	0	0	0	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	0	0	0	0
1	0	1	1	0	1	0	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	1	0
1	1	1	0	0	0	0	0
1	1	1	1	0	0	0	1

 

② Design 1:8 demux using two 1:4 demux.

Sol:  $2^n = 8 = 2^3$

$n=3$

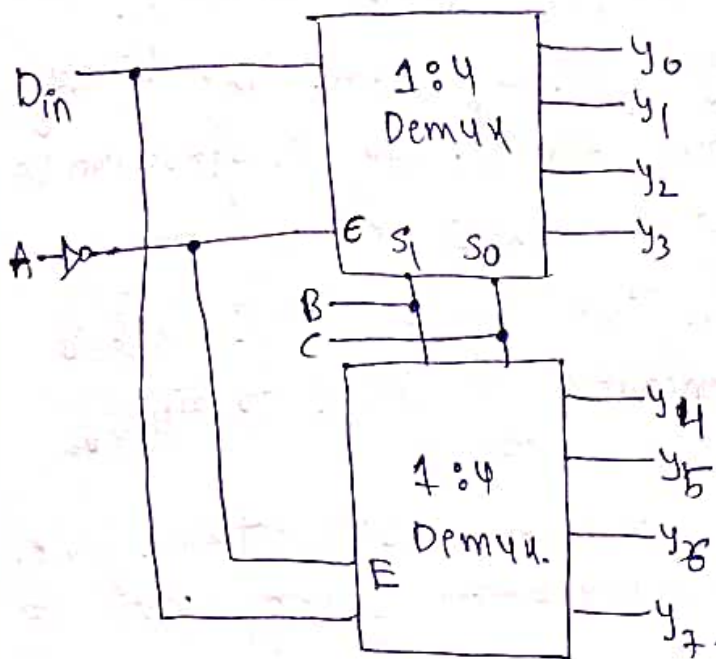


	$S_1$	$S_0$	$D_{in}$
A	B	C	
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

③ Implement full subtractor using demux

Sol: Difference  $(D) = \Sigma (1, 2, 4, 7)$   
Borrow  $(B) = \Sigma (1, 2, 3, 7)$

A	B	C	Borrow	Diff
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

 

## Encoders :-

An encoder is digital circuit that performs the inverse operation of a decoder. An encoder has  $2^n$  input lines and 'n' output lines (fewer).

The o/p lines as an aggregate generate the binary code corresponding to input lines. The encoder can be implemented with OR gates, whose inputs are directly determined from the truth table. One of the example for this encoder is Octal to Binary encoder.

① Draw Octal to Binary encoder with truth table.

Sol:-


Inputs								Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

$$x = D_4 + D_5 + D_6 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$z = D_1 + D_3 + D_5 + D_7$$



 


### Ambiguities (or) Limitations in Octal to Binary encoder:-

- (i) In this, if two inputs are active (i.e., equal to 1). Simultaneously, the o/p produce an undefined combination.
- (ii) If o/p with all zeros is generated when all the inputs are zero, but this output is seen as when  $D_0$  is equal to 1. This can be resolved by one or more o/p's to indicate whether at least one input is equal to 1.  
i.e., validate output.

### Priority Encoder:-

$D_0$	$D_1$	$D_2$	$D_3$	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

 


0010 → 2  
 0110 → 6  
 1010 → 10  
 1110 → 14

0001 → 1  
 0011 → 3  
 0101 → 5  
 0111 → 7  
 1001 → 9  
 1011 → 11  
 1101 → 13  
 1111 → 15


$$A = D_3 + D_2$$

 A priority encoder is an encoder circuit that includes priority function. The operation of the priority encoder is such that if two or more inputs equal to 1 at the same time the input having highest priority will take precedence.



0100 → 4  
 1100 → 12

$$y = D_3 + D_1 \bar{D}_2$$

 


1000 → 8

$$V = D_3 + D_2 + D_1 \bar{D}_2 + D_0 \bar{D}_2$$

(or)

$$V = D_0 + D_1 + D_2 + D_3$$

 

### Decoder:-

A decoder is a combinational circuit that converts binary information from 'n' input lines to a maximum  $2^n$  unique output lines.

If 'n' bit coded information has unused combinations the decoder may have fewer than  $2^n$  o/p's.

① Draw 3:8 line decoder, circuit with truth table or. Draw binary to octal converter.

Sol:- Binary to Octal Converter:-

i/p			o/p							
x	y	z	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

$$D_0 = x'y'z'$$

$$D_1 = x'y'z$$

$$D_2 = x'y'z'$$


$$D_3 = x'y'z$$

$$D_4 = xy'z'$$

$$D_5 = xy'z$$

$$D_6 = xy'z'$$

$$D_7 = xy'z$$

 




② Draw 2:4 line decoder with enable i/p  
Construction with NAND gate.

Soln

E	A	B	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

 


$$D_0 = A'B', D_1 = A'B, D_2 = AB', D_3 = AB$$

③ Construct 4:16 line decoder with two 3:8 line decoders and enable inputs.

Soln

A	B	C	D
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

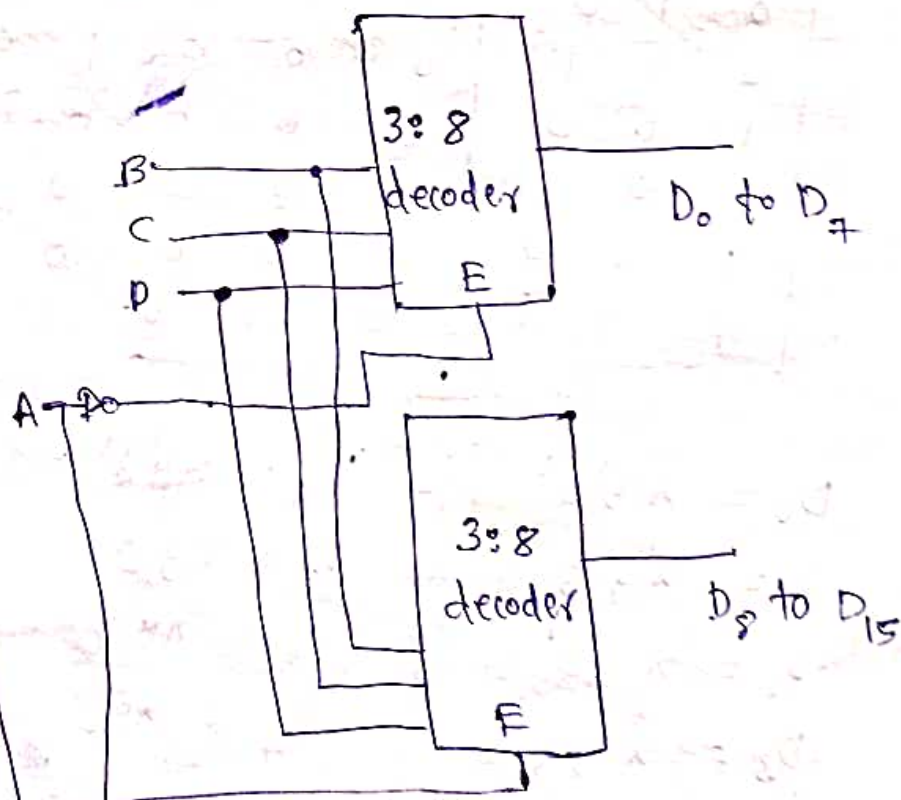

## Combinational Logic Implementation:-

A decoder provides the  $2^n$  min terms for  $n$  input variables for implementing combinational circuit by means of a decoder and OR gates required.


① Implement a full adder with a decoder.

Sol<sup>n</sup>

A	B	C	Carry	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$\text{Carry} = \Sigma (3, 5, 6, 7)$$

$$\text{Sum} = \Sigma (1, 2, 4, 7)$$

 
 
## PLDs - Programmable Logic Devices:-

PLDs are that integrated circuits (ICs). They contain an array of AND gates and another array of OR gates. There are 3 types of PLDs. Based on the type of array, which has programmable feature.



Conventional symbol of AND gate




Array Logic symbol of AND gate





Conventional Symbol of OR Gate.

 


Array Logic Symbol of OR Gate.

The programming is here hardware programming but not software programming. The 3 types of PLDs are


- (i) PROM - Programmable Read Only Memory
- (ii) PAL - Programmable Array Logic
- (iii) PLA - Programmable Logic Array.

The basic configurations of 3 PLDs are


PROM:

 

PAL:

 


PLA:

 



① Draw internal logic of a  $32 \times 8$  ROM.

Soln

 


② Implement the following Boolean functions in the PLA.

$$F_1 = AB' + AC + A'BC', \quad F_2 = (AC + BC)'$$

Soln

Product term	I/P			O/P	
	A	B	C	$F_1(T)$	$F_2(C)$
$AB'$	1	0	-	1	-
$AC$	1	-	1	1	1
$BC$	-	1	1	-	1
$A'BC'$	0	1	0	1	-

Programming Table

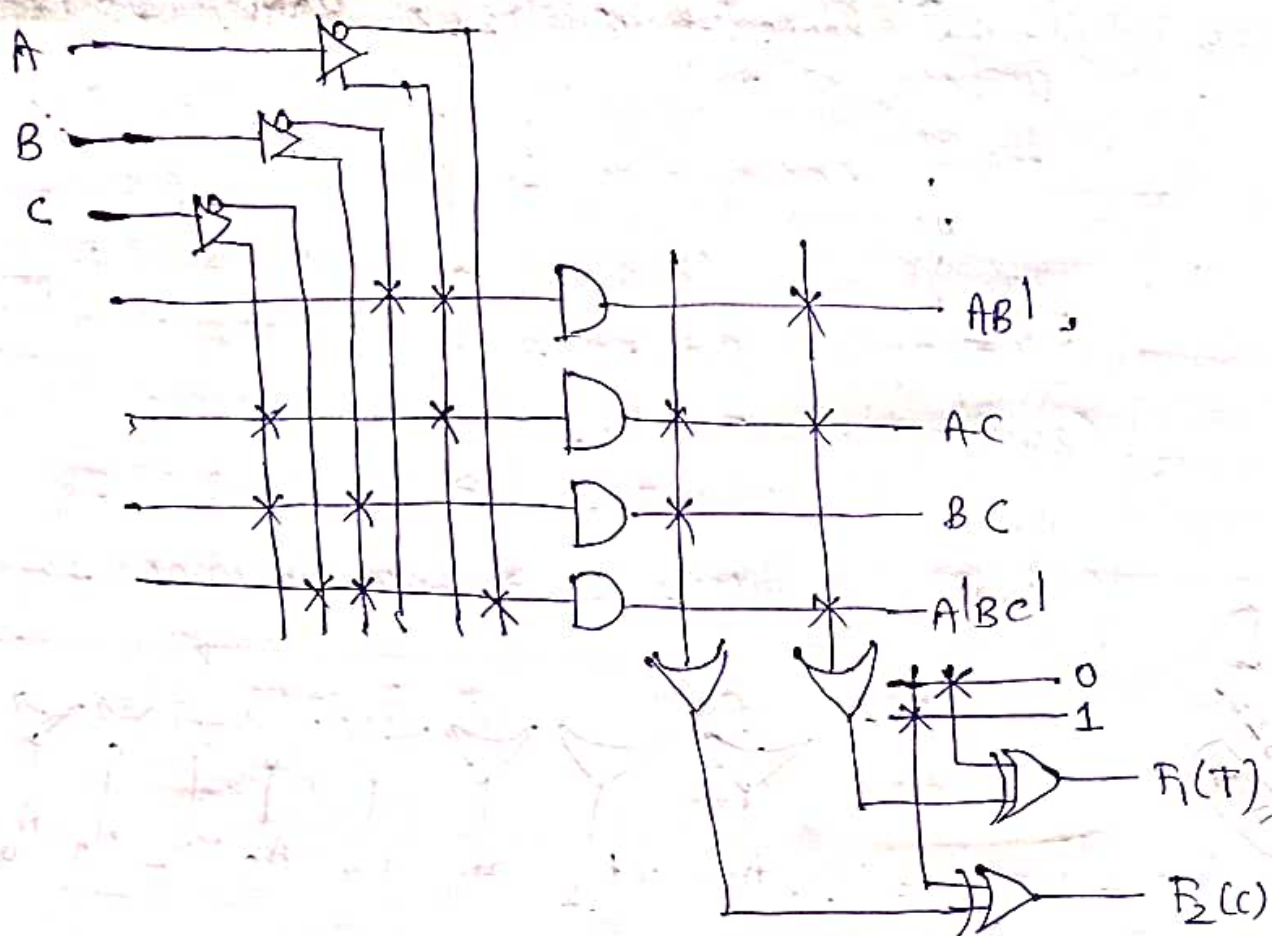

③ Implement the following two boolean functions with a PLA.

$$F_1(A, B, C) = \sum (0, 1, 2, 4)$$

$$F_2(A, B, C) = \sum (0, 5, 6, 7)$$

Sol: given,  $F_1(A, B, C) = \sum (0, 1, 2, 4)$

A \ BC				
	00	01	11	10
0			0	
1		0	0	0

01	11
11	11
BC	AC

101	111
111	110
AC	AB

111	110
110	110
AB	AB

$$F_1'(A, B, C) = BC + AC + AB$$


$$F_1(A, B, C) = (BC + AC + AB)' \rightarrow (1)$$

A \ BC				
	00	01	11	10
0		0	0	0
1	0			

$$F_2'(A, B, C) = A'C + A'B + AB'C$$

$$F_2(A, B, C) = (A'C + A'B + AB'C)' \rightarrow (2)$$


$$F_1(A, B, C) = \sum (0, 1, 2, 4)$$

 

$$\begin{array}{r} 000 \\ 100 \\ \hline B'C' \end{array} \quad \begin{array}{r} 001 \\ 000 \\ \hline A'B' \end{array} \quad \begin{array}{r} 000 \\ 010 \\ \hline A'C' \end{array}$$

$$F_1(A, B, C) = B'C' + A'B' + A'C' \rightarrow (3)$$

$$F_2(A, B, C) = \sum (0, 5, 6, 7)$$

 


$$\begin{array}{r} 101 \\ 111 \\ \hline AC \end{array} \quad \begin{array}{r} 111 \\ 110 \\ \hline AB \end{array} \quad \begin{array}{r} 000 \\ 000 \\ \hline A'B'C' \end{array}$$

$$F_2(A, B, C) = AC + AB + A'B'C' \rightarrow (4)$$

Now,  $F_1(A, B, C) = (AB + BC + AC)'$   
 $F_2(A, B, C) = AC + AB + A'B'C'$  from (1) & (4)

	Product term	I/P			O/P	
		A	B	C	$F_1(C)$	$F_2(T)$
AB	1	1	1	—	1	1
BC	2	—	1	1	1	—
AC	3	1	—	1	1	1
$A'B'C'$	4	0	0	0	—	1

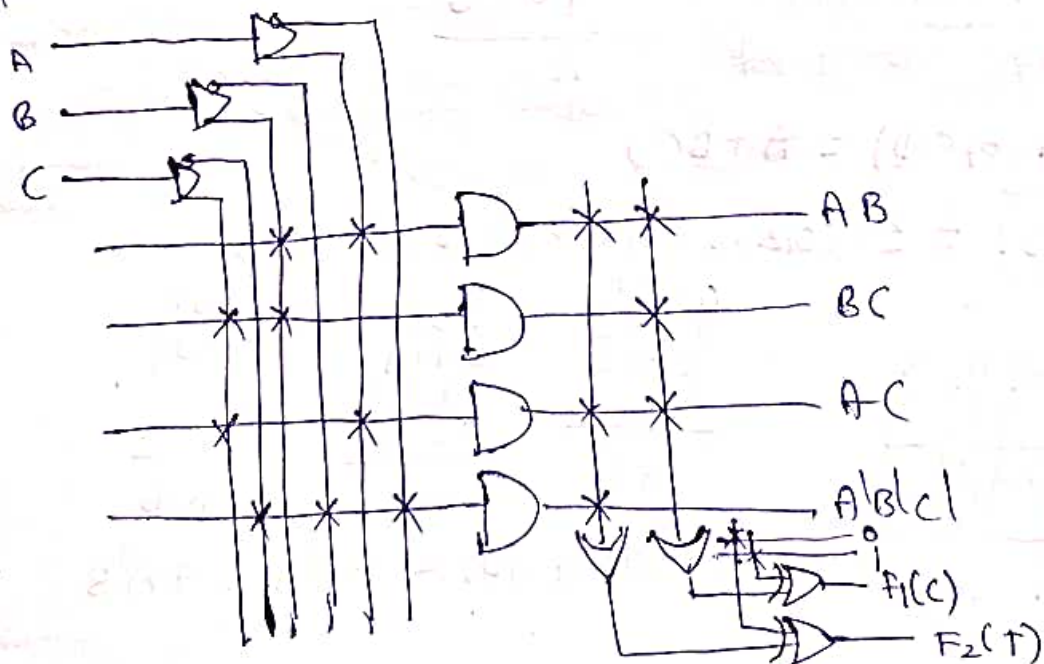



④ By using PAL design a combinational circuit by considering the following boolean functions given in sum of min terms form

$$W(A, B, C, D) = \sum (2, 12, 13)$$

$$X(A, B, C, D) = \sum (7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$Y(A, B, C, D) = \sum (0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$$

$$Z(A, B, C, D) = \sum (1, 2, 8, 12, 13)$$

Sol:  $W(A, B, C, D) = \sum (2, 12, 13)$

AB \ CD				
	00	01	11	10
00				1
01				
11	1			
10				

$$\begin{array}{r} 1100 \\ 1101 \\ \hline ABC' \end{array}$$

$$\begin{array}{r} 0010 \\ \hline A'B'CD' \end{array}$$

$$\therefore W(A, B, C, D) = ABC' + A'B'CD'$$

$$X(A, B, C, D) = \sum (7, 8, 9, 10, 11, 12, 13, 14, 15)$$

AB \ CD				
	00	01	11	10
00				
01				
11	1	1	1	1
10	1	1	1	1

$$\begin{array}{r} 1100 \\ 1101 \\ 1111 \\ 1110 \\ 1000 \\ 1001 \\ 1011 \\ 1010 \\ \hline A \end{array}$$

$$\begin{array}{r} 0111 \\ 1111 \\ \hline BCD \end{array}$$

$$\therefore X(A, B, C, D) = A + BCD$$

$$Y(A, B, C, D) = \sum (0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$$

AB \ CD				
	00	01	11	10
00	1		1	1
01	1	1	1	1
11				1
10	1		1	1

$$\begin{array}{r} 0000 \\ 1000 \\ 0010 \\ 1010 \\ \hline B'D' \end{array}$$

$$\begin{array}{r} 0011 \\ 0111 \\ 1111 \\ 1011 \\ \hline CD \end{array}$$

$$\begin{array}{r} 0100 \\ 0101 \\ 0111 \\ 0110 \\ \hline A'B \end{array}$$

$$\therefore Y(A, B, C, D) = B'D' + CD + A'B$$

$$Z(A, B, C, D) = \sum (1, 2, 8, 12, 13)$$

AB \ CD	CD			
	00	01	11	10
00		1		1
01				
11	1	1		
10	1			

$$\frac{0001}{A'B'C'D}$$

$$\frac{0010}{A'B'C'D}$$

$$\frac{1100}{A'BC'D}$$

$$\frac{1000}{A'CD}$$

$$Z(A, B, C, D) = A'B'C'D + A'B'C'D' + ABC'D + A'CD'$$

$$Z(A, B, C, D) = W + A'CD' + A'B'C'D$$

Programming Table.

Product Term	Inputs					Outputs			
	A	B	C	D	W	W	X	Y	Z
1. $ABC'D$	1	1	0	-	-	1	-	-	-
2. $A'B'CD'$	0	0	1	0	-	1	-	-	-
3. $A$	1	-	-	-	-	-	1	-	-
4. $BCD$	-	1	1	1	-	-	1	-	-
5. $W$	-	-	-	-	1	-	-	-	1
6. $A'CD'$	1	-	0	0	-	-	-	-	1
7. $A'B'C'D$	0	0	0	1	-	-	-	-	1
8. $B'D'$	-	0	-	0	-	-	-	1	-
9. $CD$	-	-	1	1	-	-	-	1	-
10. $A'B$	0	1	-	-	-	-	-	1	-

A A' B B' C C' D D' w w'

