
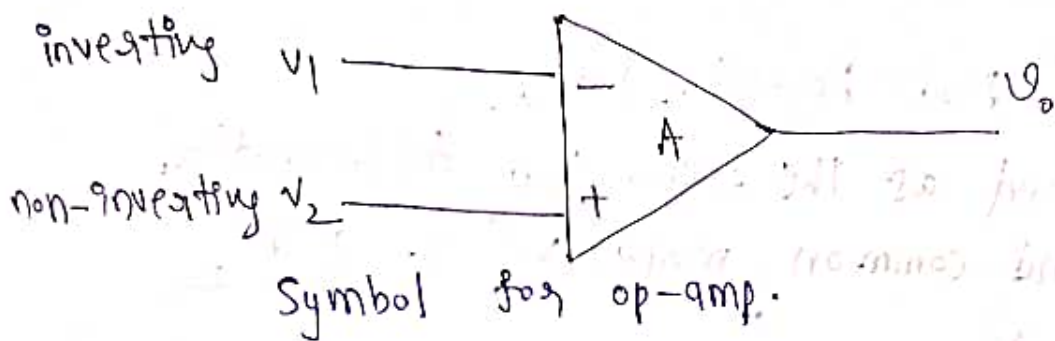


Operational Amplifier

29/Mar/2022.


Block diagram of op-amp:-

Op-amp means operational amplifiers.

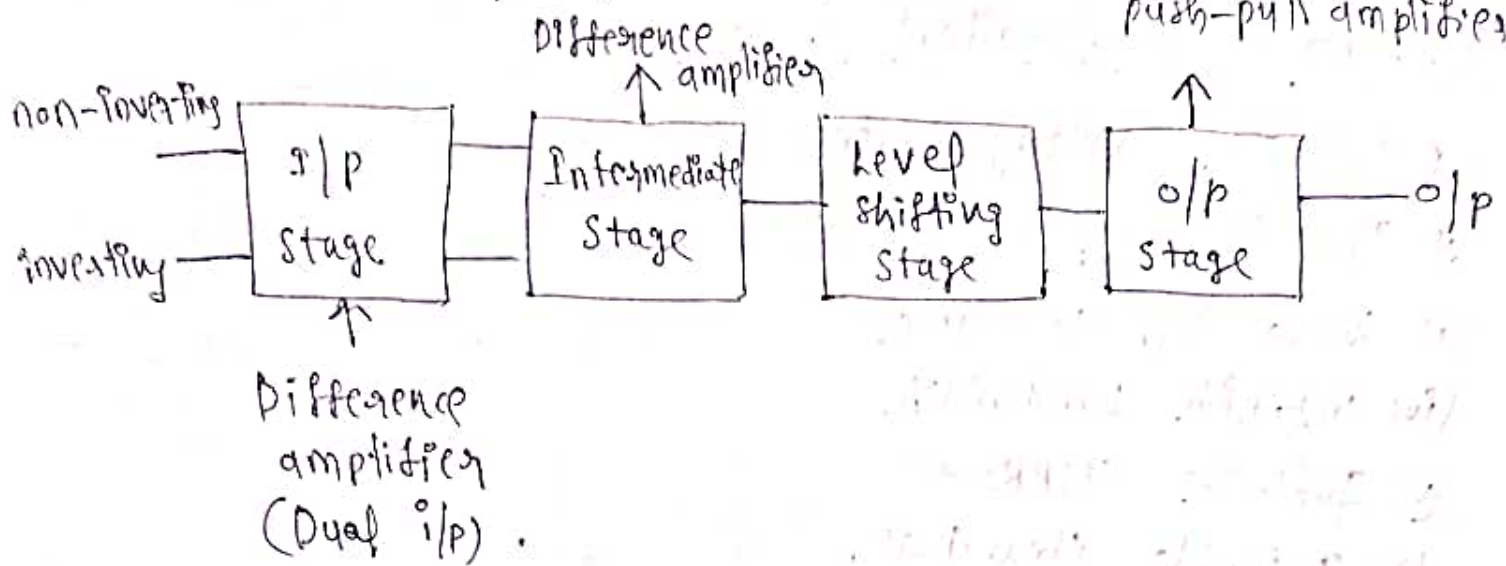

A = Gain of the amplifiers.

Pin configuration of 741 op-amp:-

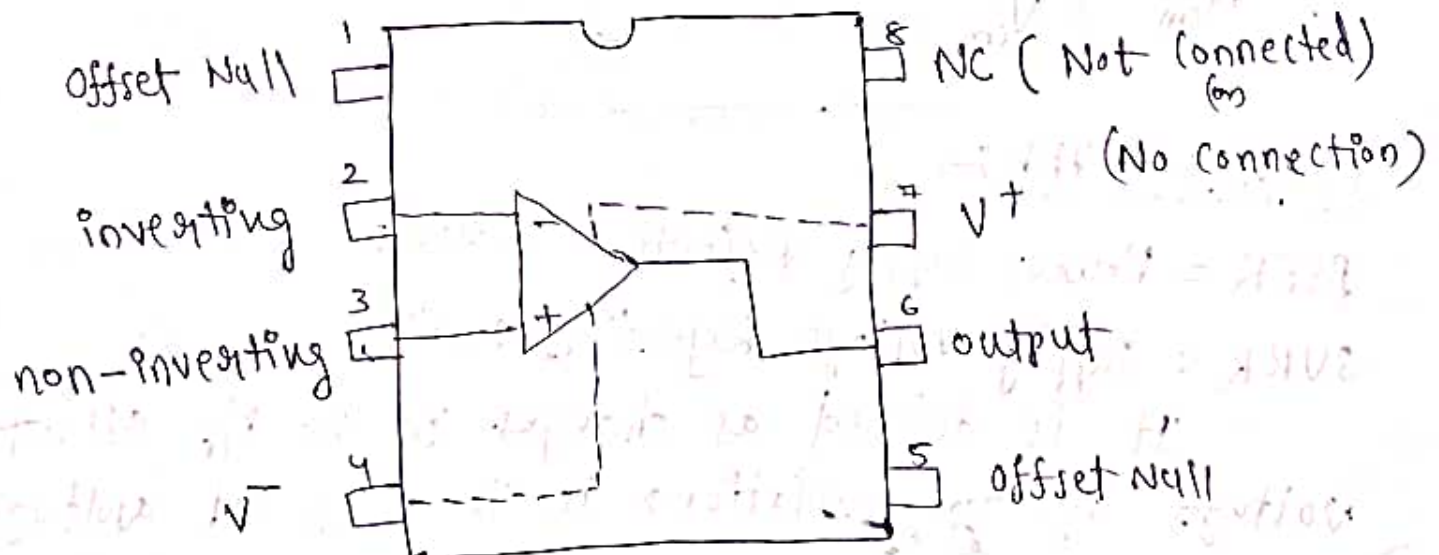

Offset Null (0) :-

The voltage applied to get o/p zero.

MOS = Metal Oxide Semiconductor

Characteristics of ideal op-amp :-

- (i) Infinite voltage gain.
- (ii) Infinite i/p resistance.
- (iii) Zero o/p resistance.
- (iv) Infinite bandwidth.
- (v) Infinite CMRR
- (vi) Infinite Slew Rate.


CMRR :-

CMRR = Common Mode Rejection Ratio.

It is defined as the ratio b/w differential voltage gain and common mode voltage gain.

$$CMRR = \frac{A_d}{A_{cm}}$$

$$A_{cm} = \frac{V_{ocm}}{V_{cm}}$$

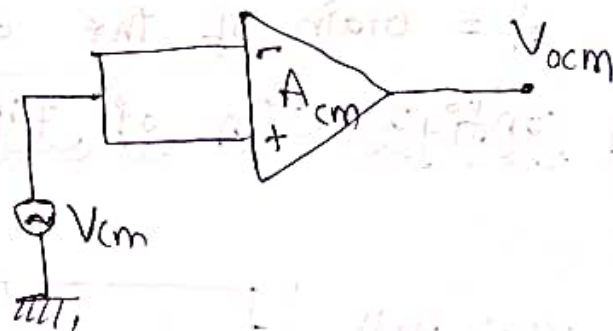

PSRR & SVRR :-

PSRR = Power Supply Rejection Ratio.

SVRR = supply voltage Rejection Ratio.

It is defined as changes in the i/p offset voltage due to variations in the supplied voltage.

$$PSRR = \frac{\Delta V_{io}}{\Delta V}$$

V_{io} = input offset voltage.



Offset voltage ಅಂತರವು ಶೂನ್ಯವಾಗಿರಬೇಕು.

Slew Rate

It is defined as maximum rate of change of o/p voltage per unit of time. It is measured in volts / microsecond.

$$SR = \left. \frac{dV_o}{dt} \right|_{\max} \text{ in } V/\mu s.$$

741 op-amp & slew rate = $0.5 V/\mu s$.

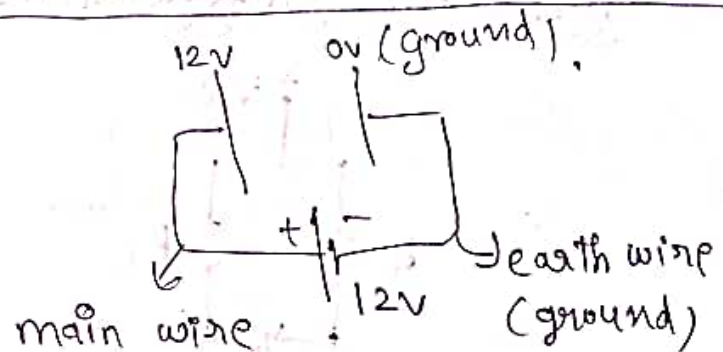
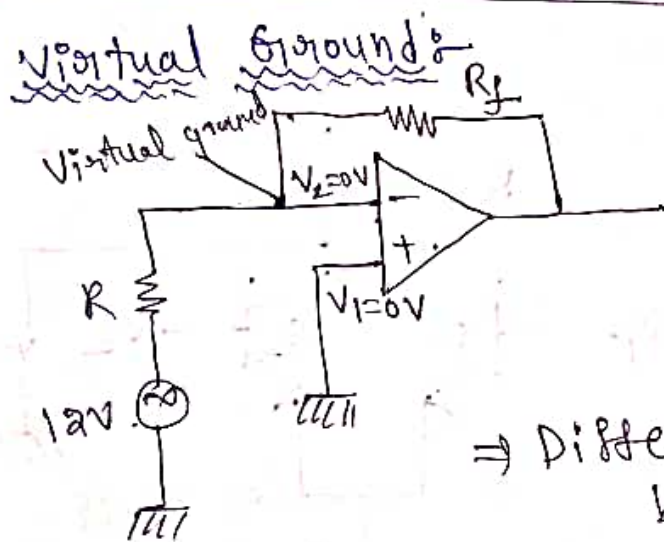


⇒ Difference in i/p voltages must be zero.

$$V_1 - V_2 = 0 \Rightarrow V_1 = V_2.$$

if $V_1 = 0$, $V_2 = 0$


Differential Amplifier Configurations

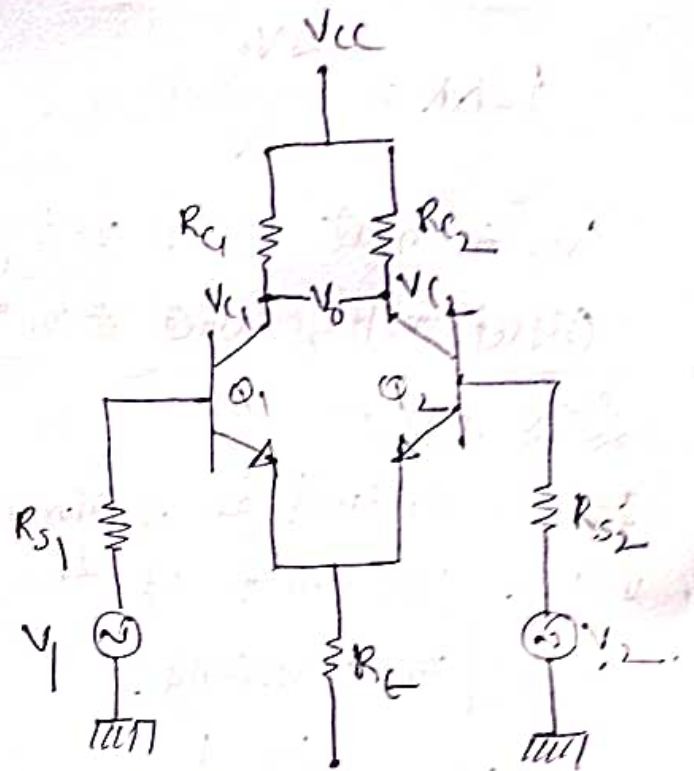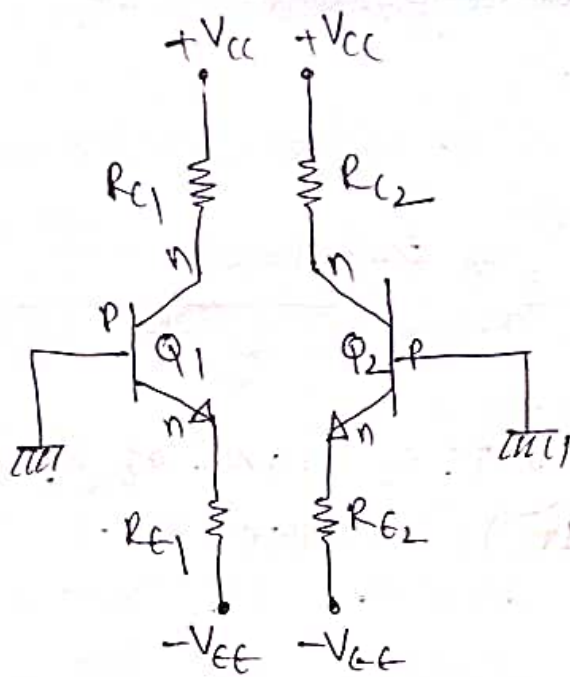


\Rightarrow if $V_1 > V_2$ then $V_O = +V_E$ (positive)

$$V_{C1} - V_{C2} = V_O$$


Different Configurations

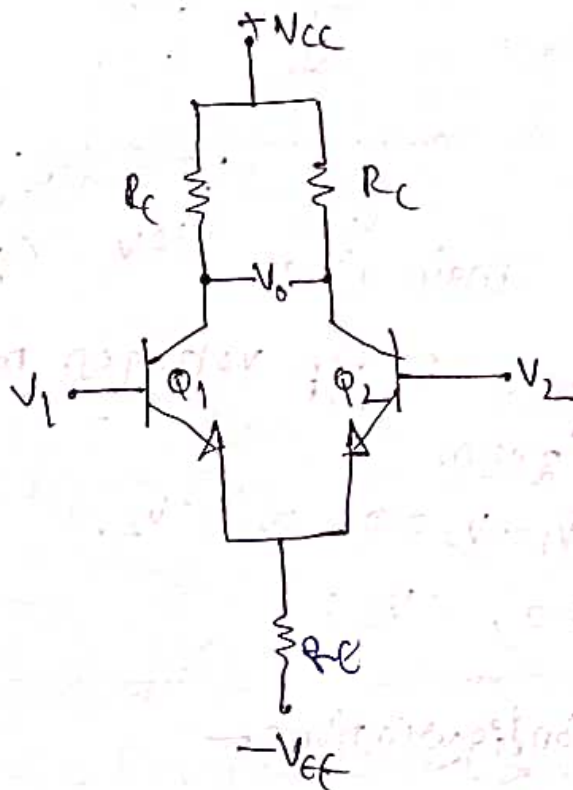

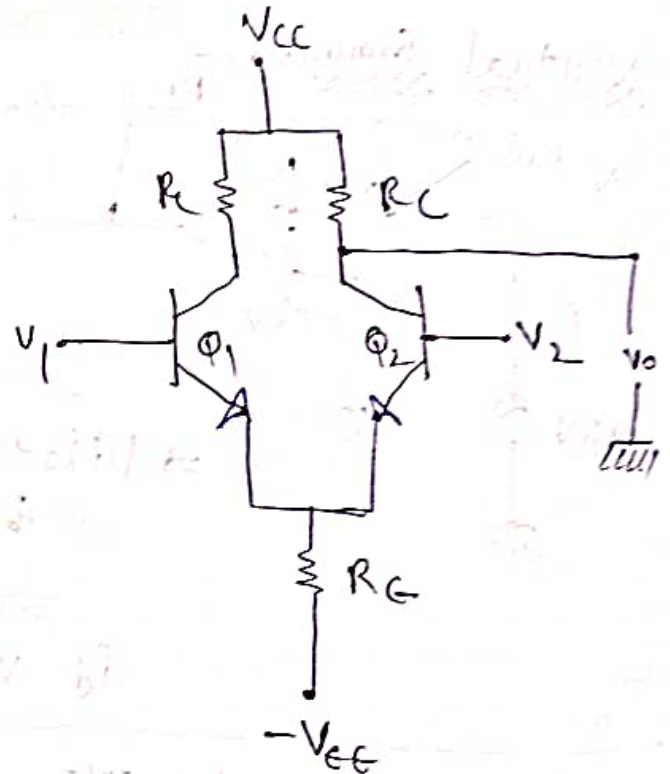
(i) Dual input balanced o/p differential amplifier.



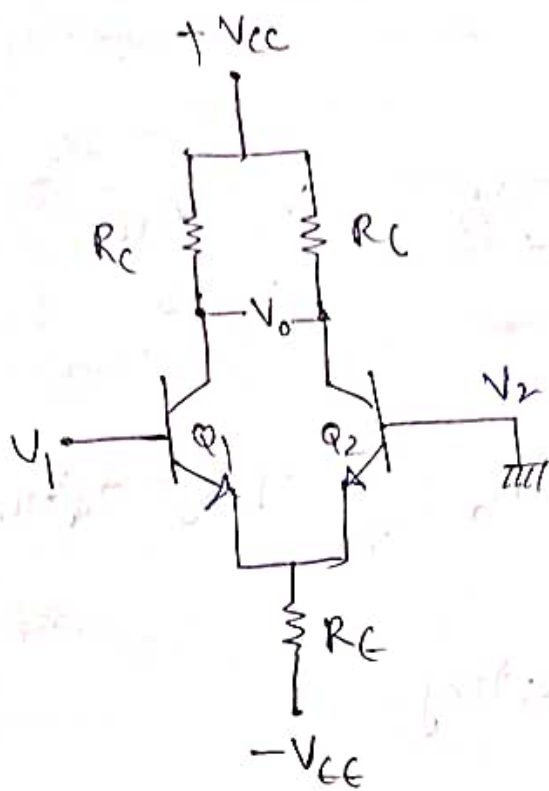(ii) Dual i/p unbalanced o/p differential amplifier.



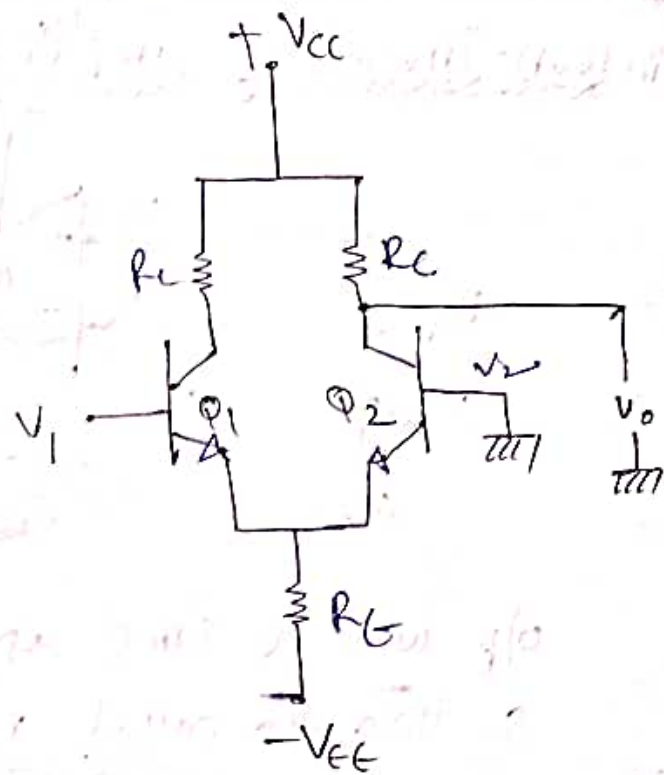(iii) Single i/p balanced o/p differential amplifier.



(iv) Single i/p unbalanced o/p differential amplifier.

Applications of op-amp:-

(i) Inverting amplifier:-

$V_{in} \rightarrow$ i/p voltage

$R_{in} \rightarrow$ i/p resistance

$A_d =$ gain of amplifier.


$V_o =$ o/p voltage.

$V_2 = V_{in}$, $V_1 = 0$.

$$A_d = \frac{-V_o}{V_{in}}$$


$$V_o = -A_d V_{in}$$

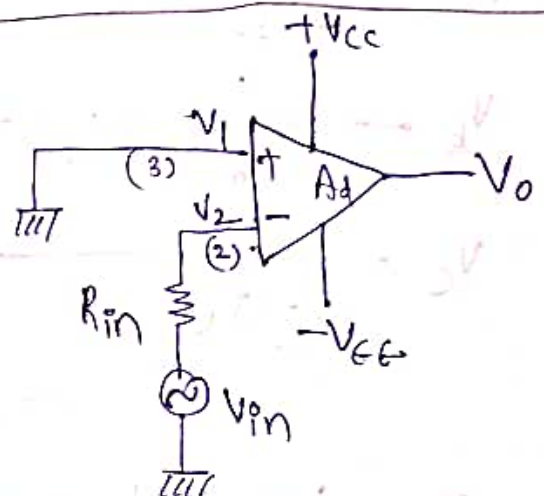\Rightarrow o/p will be -ve of the i/p. so this is called inverting amplifier.



$$A_d = \frac{V_{o/p}}{V_{i/p}}$$

(ii) Non-inverting amplifiers

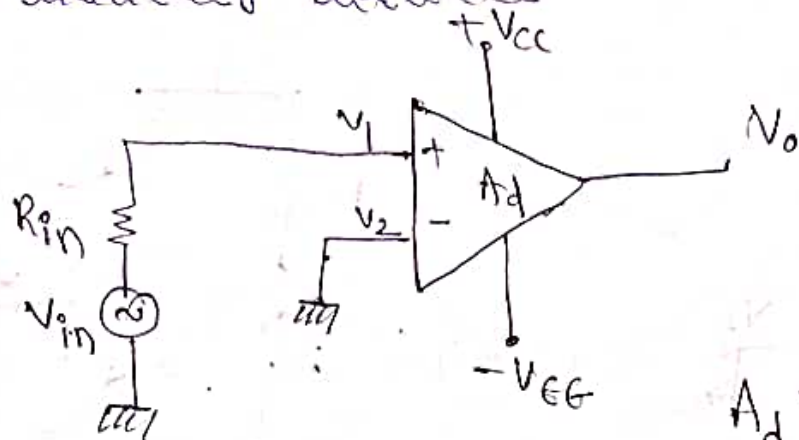

$$V_1 = V_{in}$$


$$V_2 = 0$$

$$A_d = \frac{V_o}{V_{in}} \Rightarrow V_o = A_d V_{in}$$

o/p will be same as i/p.

So this is called non-inverting.

(iii) Summing Amplifier

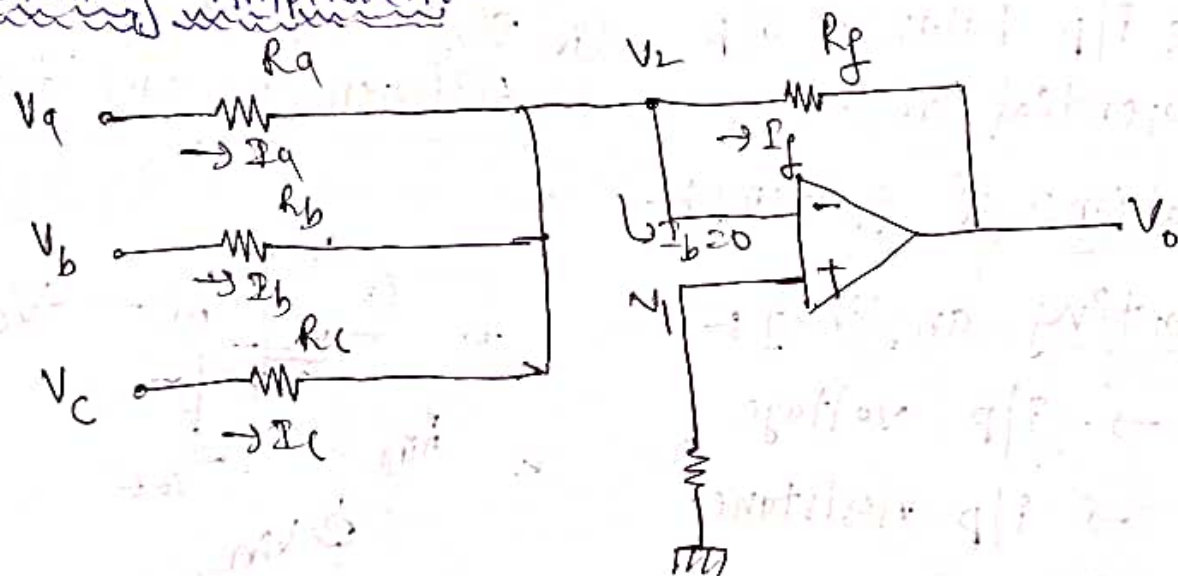

I_f = feed back current.

by applying KCL at V_2 node.

$$I_a + I_b + I_c = I_f + I_b$$

$$I_b = 0 \Rightarrow I_a + I_c = I_f$$

$$\frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c} = \frac{-V_o}{R_f}$$

$$V_o = -R_f \left(\frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c} \right)$$


Let $R_a = R_b = R_c = R$

$$V_o = -R_f \left(\frac{V_a + V_b + V_c}{R} \right)$$

$\frac{R_f}{R}$ is the gain of the amplifier.

if $\frac{R_f}{R} = 1$ then $V_o = -(V_a + V_b + V_c)$

(iv). Difference Amplifier

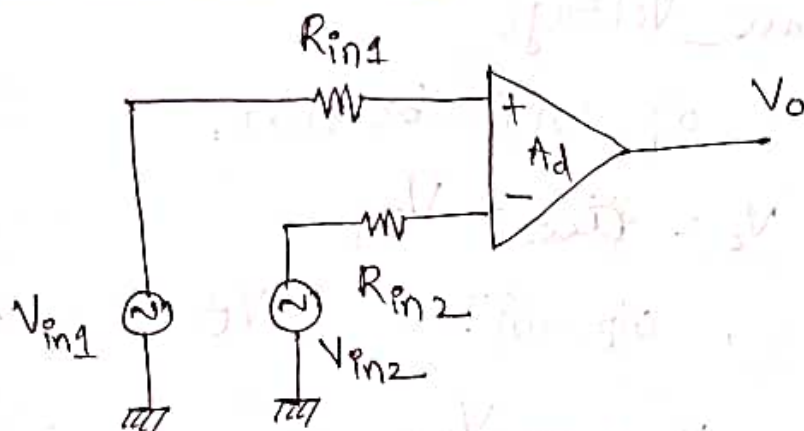


Applications


$$V_o = A_d (V_{in1} - V_{in2})$$

$$A_d = \frac{\text{o/p voltage}}{\text{i/p voltage}} = \frac{V_{o/p}}{V_{i/p}}$$

A_d = differential gain.

(v). Comparator

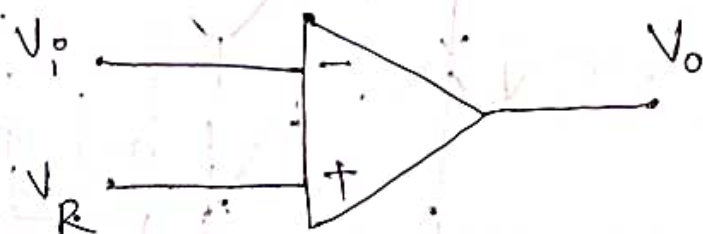

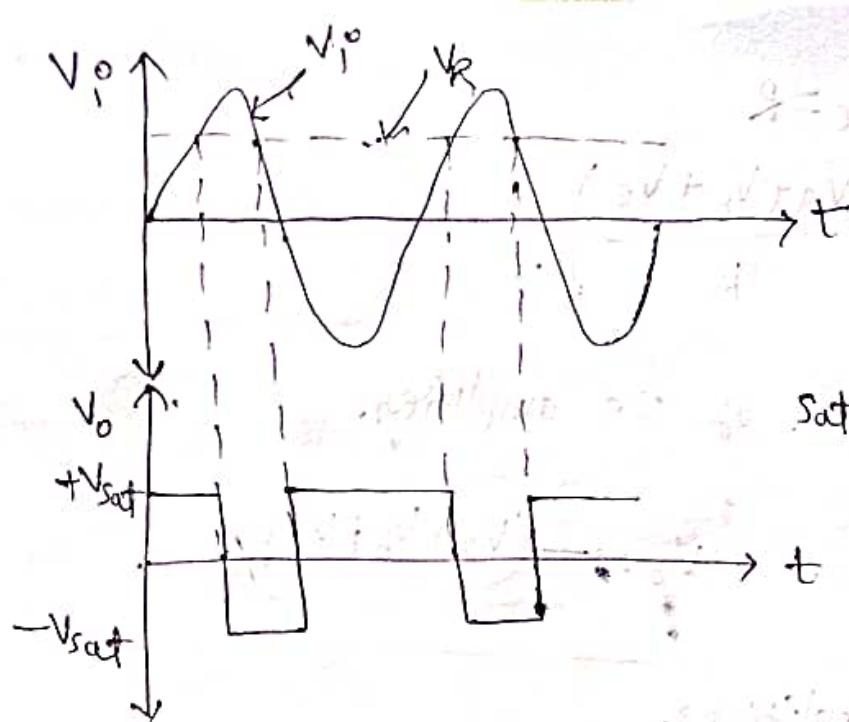

V_{sat} = Saturation.

V_R = Reference Voltage


(i) If $V_i < V_R$, o/p. will be $+V_e$.

$$V_o = +V_{sat}$$

(ii) If $V_i > V_R$, o/p. will be $-V_e$.

$$V_o = -V_{sat}$$

(vi) Differentiator:-

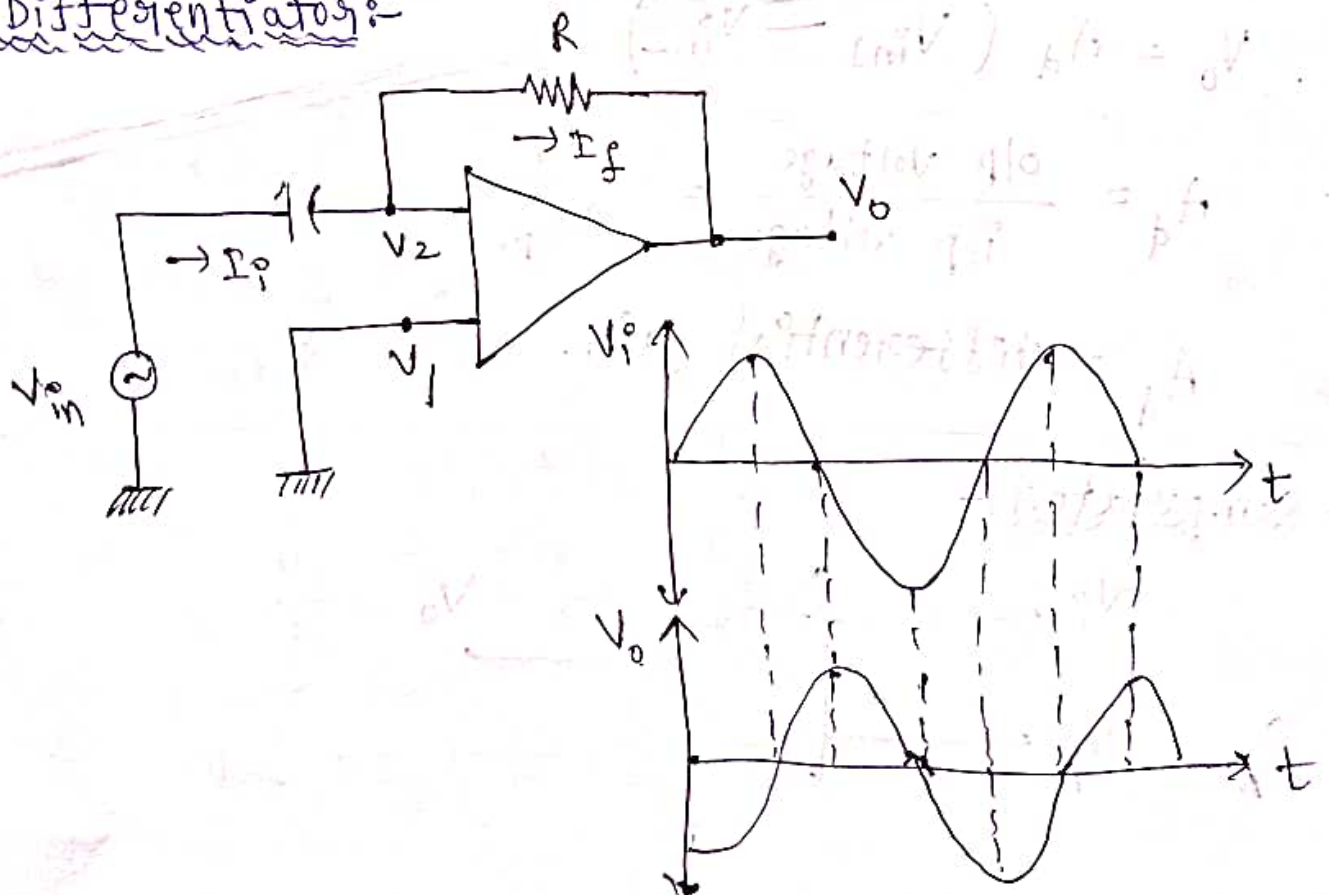

$$\Rightarrow I_i = I_f$$

$$I_i = I_b + I_f$$

wekt, $I = C \cdot \frac{dV}{dt}$

Here, $I_b = 0$

$$I_i = I_f$$


$$C \cdot \frac{d}{dt} (V_{in} - V_2) = \frac{V_2 - V_o}{R}$$

But $V_2 = 0 \downarrow$ virtual ground,


$$C \cdot \frac{d}{dt} V_{in} = \frac{-V_o}{R}$$

$$V_o = -RC \frac{d}{dt} (V_{in})$$

$RC = \text{Time Constant}$

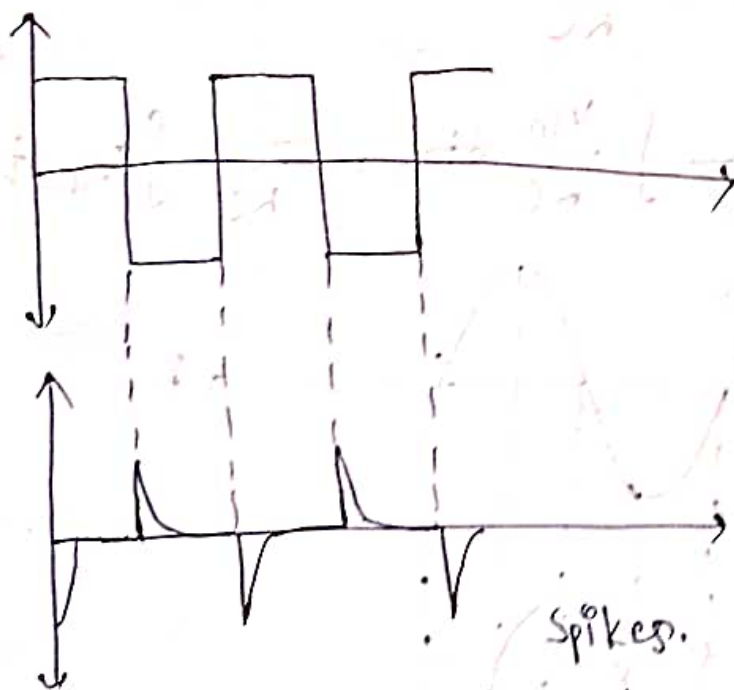

(vii) Integration:

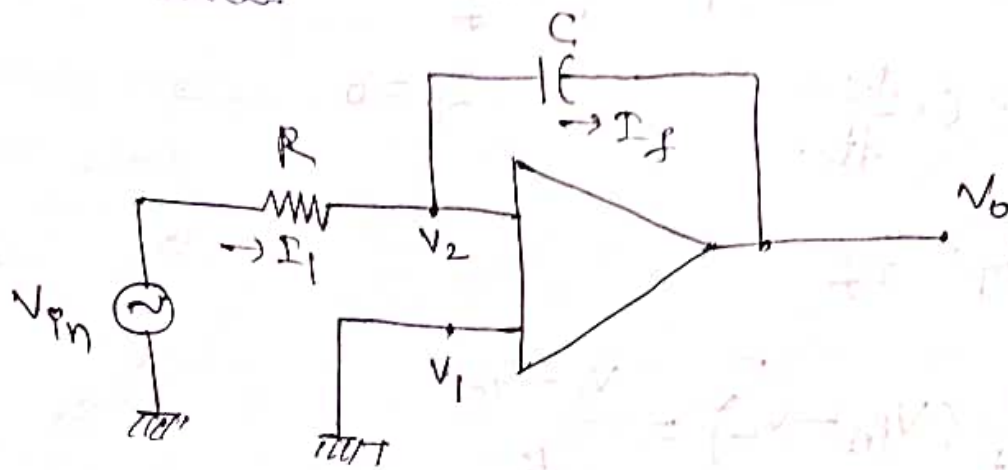

$$I_1 = I_f$$


$$\frac{V_{in} - V_2}{R} = C \frac{d}{dt} (V_2 - V_o)$$


$$\Rightarrow V_2 = 0.$$

$$\frac{V_{in}}{R} = C \cdot \frac{d}{dt} (-V_o)$$


$$-\frac{d}{dt} V_o = \frac{V_{in}}{RC}$$
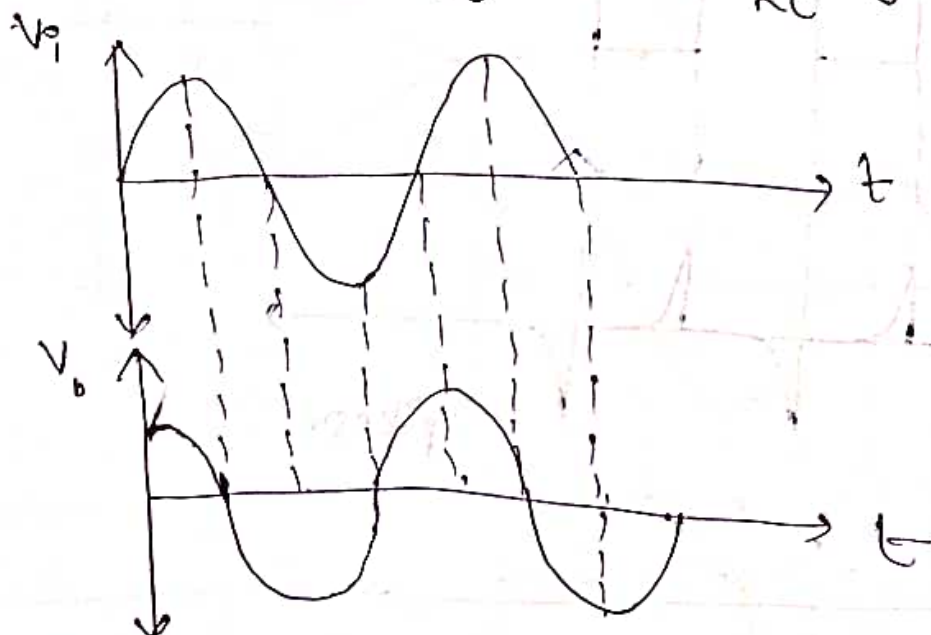
$$V_o = - \int \frac{V_{in}}{RC} dt = -\frac{1}{RC} \int V_{in} dt.$$



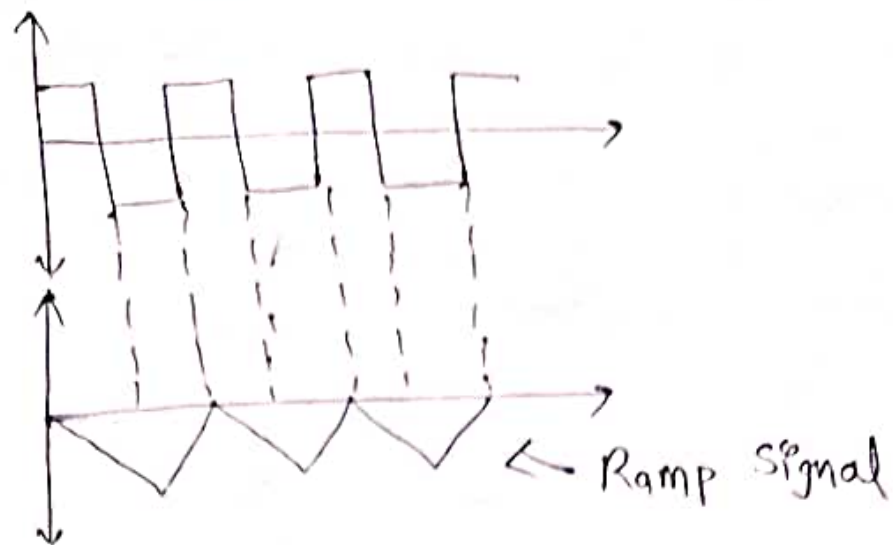

(viii) Voltage Follower:-

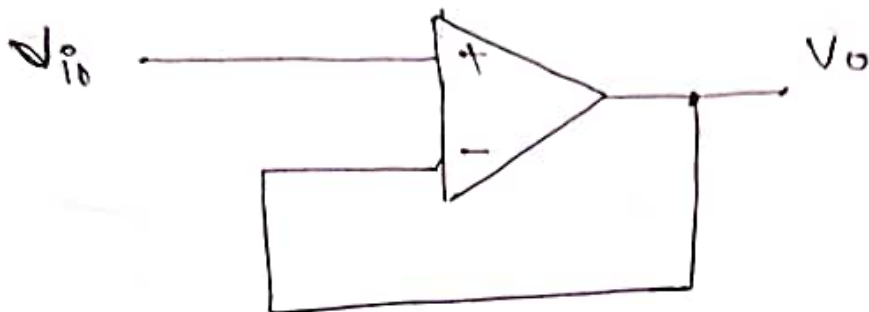

-ve feedback,

$$A_d = \text{Gain} = \text{Unity} = 1.$$

$$V_o = A_d V_{in} \quad \downarrow \quad A_d = 1$$

$$\boxed{V_o = V_{in}}$$